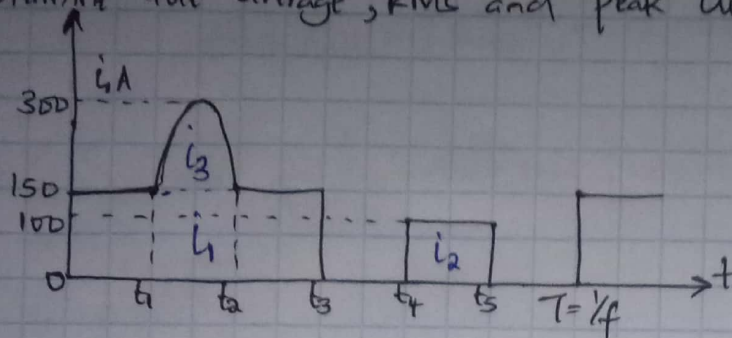


Name: Shiranga Aka Eddmand ; Adm No: TLE/19/15.
 Task: CATA Take Away.
 Course: ECE 451 by Dr. Letting.

Question ONE.

The waveform of the current flowing through a diode are as shown below.
 Determine the average, RMS and Peak current ratings of the diode.



$$\begin{aligned} t_1 &= 100 \mu\text{s} \\ t_2 &= 200 \mu\text{s} \\ t_3 &= 400 \mu\text{s} \\ t_4 &= 800 \mu\text{s} \\ t_5 &= 1 \text{ ms} \\ f &= 200 \text{ Hz} \\ T &= 1/200 = 5 \times 10^{-3} \end{aligned}$$

Soln:

$$i_1 = \frac{t_3 - 0}{T} \times 150 = \frac{400 \times 10^{-6}}{5 \times 10^{-3}} \times 150 = 12 \text{ A}$$

$$i_2 = \frac{t_5 - t_4}{T} \times 100 = \frac{10^{-3} - 800 \times 10^{-6}}{5 \times 10^{-3}} \times 100 = 4 \text{ A}$$

$$i_3 = \left[\frac{1}{\pi} \int_0^{\pi} 150 \sin \theta d\theta \right] \times \frac{t_2 - t_1}{T} = 95.49 \times \frac{100 \times 10^{-6}}{5 \times 10^{-3}} = 1.90986 \approx 1.91$$

$$i_{av} = i_1 + i_2 + i_3 = 12 + 4 + 1.91 = 17.91 \text{ A}$$

$$i_{rms} = I_{rms} = \sqrt{i_{1rms}^2 + i_{2rms}^2 + i_{3rms}^2}$$

$$i_{1rms} = 150 \times \sqrt{\frac{t_3}{T}} = 150 \times \sqrt{\frac{400}{5000}} = 42.43 \text{ A}$$

$$i_{3rms} = \frac{I_m}{\sqrt{2}} \times \sqrt{\frac{t_2 - t_1}{T}} = \frac{150}{\sqrt{2}} \times \sqrt{\frac{100}{5000}} = 15 \text{ A}$$

$$i_{2rms} = 100 \times \sqrt{\frac{t_5 - t_4}{T}} = 100 \times \sqrt{\frac{200}{5000}} = 20 \text{ A}$$

$$I_{rms} = \sqrt{42.43^2 + 15^2 + 20^2} = 49.25 \text{ A}$$

$$I_p = 300 \text{ A}$$

Question Two

i) Determine the total RMS Current Magnitude $I(A)$

$$\text{Total } I_{\text{rms}} = \sqrt{I_{1\text{rms}}^2 + I_{2\text{rms}}^2}$$

$$I_{1\text{rms}} = 10 \times \sqrt{\frac{T/2 - T/4}{T}} = 5A$$

$$I_{2\text{rms}} = -10 \times \sqrt{\frac{T - 3/4 T}{T}}$$

$$\text{Total } I_{\text{rms}} = \sqrt{5^2 + 5^2} = 7.071A$$

ii) Determine the fundamental RMS Current Magnitude $I_1 A$.

$$I_1 = \frac{C_1}{\sqrt{2}} \quad C_1 = \sqrt{a_1^2 + b_1^2}$$

$$a_1 = \frac{1}{T} \int_0^{2\pi} i(t) \cos(\omega t) d\omega t$$

$$b_1 = \frac{1}{T} \int_0^{2\pi} i(t) \sin(\omega t) d\omega t$$

$$T = 2\pi; T/4 = \pi/2; T/2 = \pi; 3/4 T = 3\pi/2$$

$$\therefore a_1 = \frac{I}{\pi} \left[\int_{\pi/2}^{\pi} \cos \omega t d\omega t + \int_{3\pi/2}^{2\pi} -\cos \omega t d\omega t \right]$$

$$= \frac{-2I}{\pi} = \frac{-20}{\pi} = -6.366$$

$$b_1 = \frac{I}{\pi} \left[\int_{\pi/2}^{\pi} \sin \omega t d\omega t + \int_{3\pi/2}^{2\pi} -\sin \omega t d\omega t \right]$$

$$= \frac{2I}{\pi} = \frac{2 \times 10}{\pi} = 6.366$$

$$C_1 = \sqrt{6.366^2 + 6.366^2}$$

$$C_1 = 9$$

$$I_1 = \frac{9}{\sqrt{2}} = 6.366 A$$

iii) Compute the total Harmonic distortion (THD) of the current

$$THD = \left[\left(\frac{I_s}{I_1} \right)^2 - 1 \right]^{1/2}$$

$$I_s = I_1 = 6.366 A$$

$$I_s = \left[\frac{1}{\pi} \int_{\pi/2}^{\pi} I_1^2 d(\omega t) \right]^{1/2} = 7.071$$

$$THD = \left[\left(\frac{7.071}{6.366} \right)^2 - 1 \right]^{1/2}$$

$$= 0.4835$$

$$THD = \left[\left(\frac{10}{6.366} \right)^2 - 1 \right]^{1/2}$$

$$= 1.21$$

iv) Compute the Supply Power factor P.F.

$$P.F = \frac{I_{S1}}{I_S} \cos \phi$$


$$\phi = \tan^{-1} \left(\frac{a_1}{b_1} \right) = \tan^{-1} \left(\frac{-6.366}{6.366} \right)$$

$$\phi = -45^\circ$$
$$\cos(-45^\circ) = \underline{\underline{0.7071}}$$

$$P.F = \frac{6.366}{7.071} \times 0.7071$$
$$= \underline{\underline{0.64}}$$

Question THREE

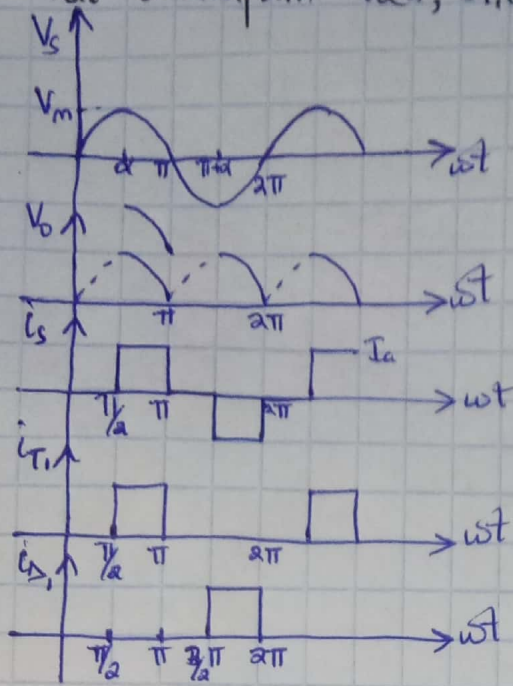a) Sketch the waveform $V_s(t)$, $i_T(t)$, $i_D(t)$ and $i_s(t)$



b) Determine the average and rms current rating of Diode D_1 and Thyristor T_1

Diode D_1 :

$$I_{av} = \frac{2\pi - \frac{3}{2}\pi}{2\pi} \times 10 = \underline{\underline{2.5A}}$$

$$I_{rms} = \left[\frac{1}{2\pi} \int_{\frac{3}{2}\pi}^{2\pi} 10^2 dt \right]^{1/2} = \underline{\underline{5A}}$$

Thyristor T_1 :

$$I_{av} = \frac{\pi - \frac{\pi}{2}}{2\pi} \times 10 = \underline{\underline{2.5A}}$$

$$I_{rms} = \left[\frac{1}{2\pi} \int_{\frac{\pi}{2}}^{\pi} 10^2 dt \right]^{1/2} = \underline{\underline{5A}}$$